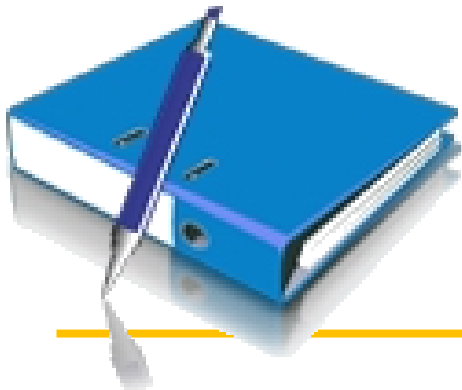
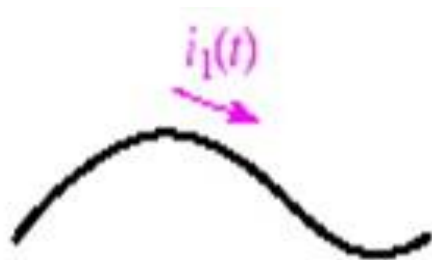

Chapter 1-9 REVIEW




Chapter 1 Basic Components and Electric Circuits

符号和数值缺一不可！




(c)

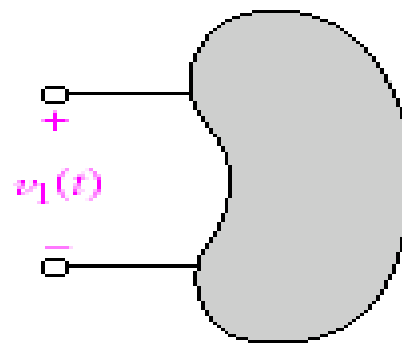

(c)

passive sign convention


关联参考方向

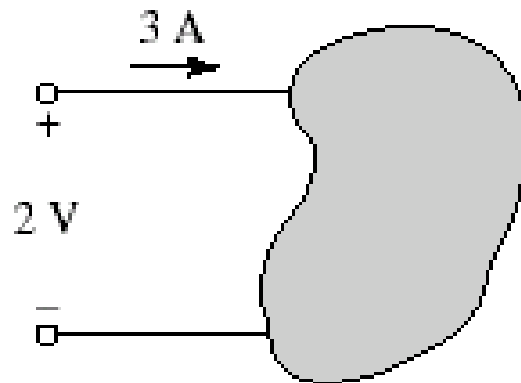


The reference current is defined **consistent with passive sign convention**（与关联参考方向一致），which assumes that the element is **absorbing power**.

Voltage and Current Sources


Independent Sources

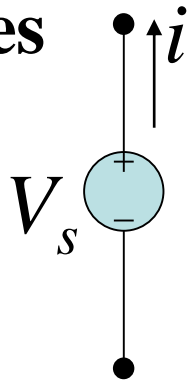


(a)

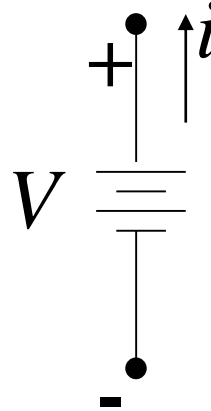


(b)

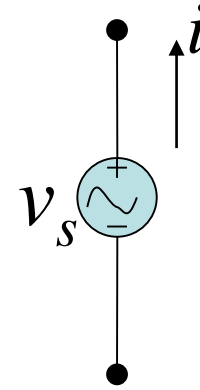


(c)

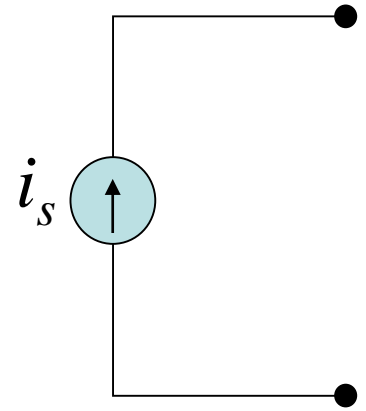


Dependent Sources

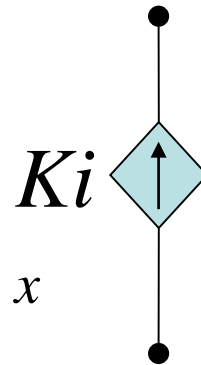


(a)

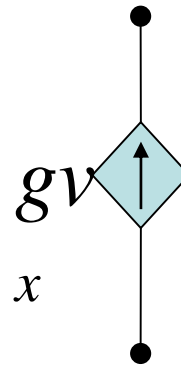

(b)

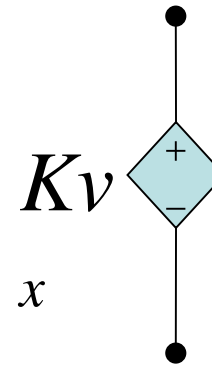

(c)


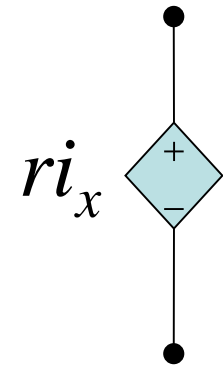


(d)

Ohm's Law

$$v = iR$$

$$p = vi = i^2 R = v^2 / R$$

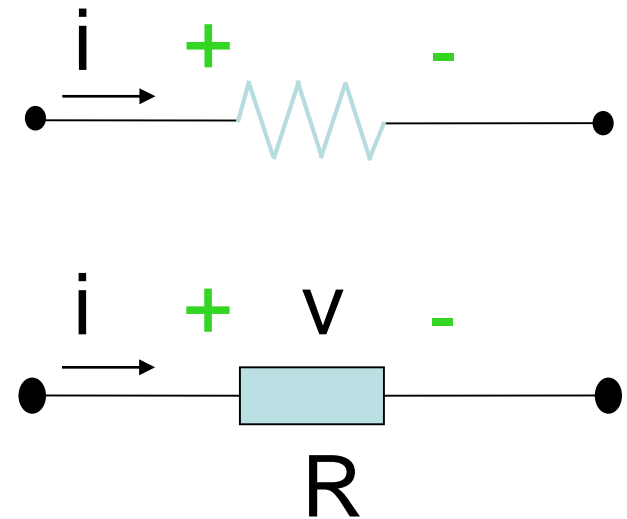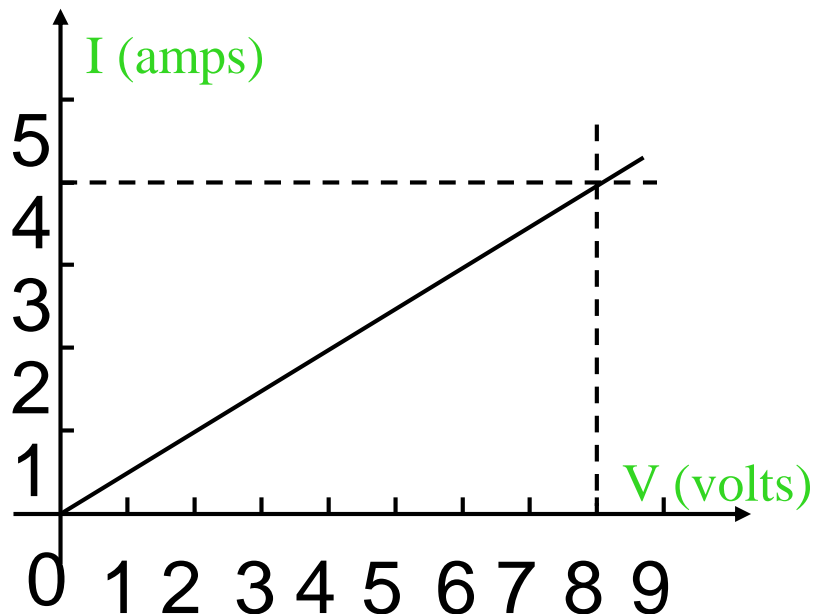

Circuit symbol for
the resistor

Chapter 2 Voltage and Current Laws

- Ability to employ Kirchhoff's current law (**KCL**)

$$\sum_{n=1}^N i_n = 0$$

$$i_1 + i_2 + i_3 + \Lambda + i_N = 0$$

the N current arrows are either all directed toward the node in question, or are all directed away from it.

- Ability to employ Kirchhoff's voltage law (**KVL**)


$$\sum_{n=1}^N v_n = 0$$

$$v_1 + v_2 + v_3 + \Lambda + v_N = 0$$

the algebraic sum of the voltages across the individual elements around any closed path must be zero.

Chapter 2 Voltage and Current Laws

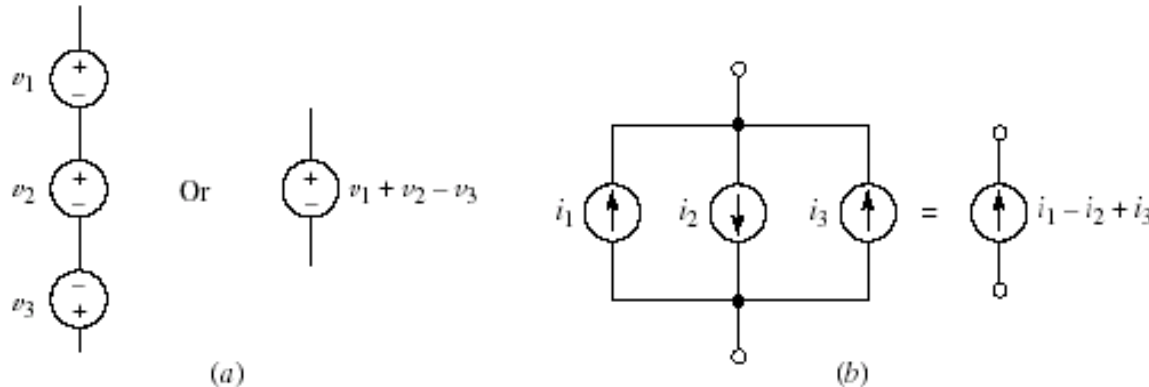- Simplify series and parallel connected sources. (电源的串并联简化)



- Reduce series and parallel resistor combinations (电阻的串并联简化)

$$R_{eq} = R_1 + R_2 + R_3 + \Lambda + R_N$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \Lambda + \frac{1}{R_N}$$

- Intuitive understanding of voltage and current division
(理解对分压/分流的概念)

Chapter 3 Basic Nodal and Mesh Analysis

◆ Implementation of nodal analysis(结点法)


- Choose one of the nodes as a reference node. Then **label** the node voltage v_1, v_2, \dots, v_{N-1} , remembering that each is understood to be measured with respect to the reference node.
- If the circuit contains **only current sources**, apply **KCL** at each nonreference node.
- If the circuit **contains voltages sources**, form a **supernode** about each one, and then proceed to apply KCL at all nonreference nodes and supernodes.

◆ Implementation of mesh analysis(网孔法)

- First make certain that the network is a planar network. **Assign a clockwise** mesh current in each mesh: i_1, i_2, \dots, i_M .
- If the circuit contains **only voltage sources**, apply **KVL** around each mesh.
- If the circuit **contains current sources**, create a supermesh for each one that is common to two meshes, and then apply KVL around each mesh and supermesh.


Chapter 4 Useful Circuit Analysis Techniques

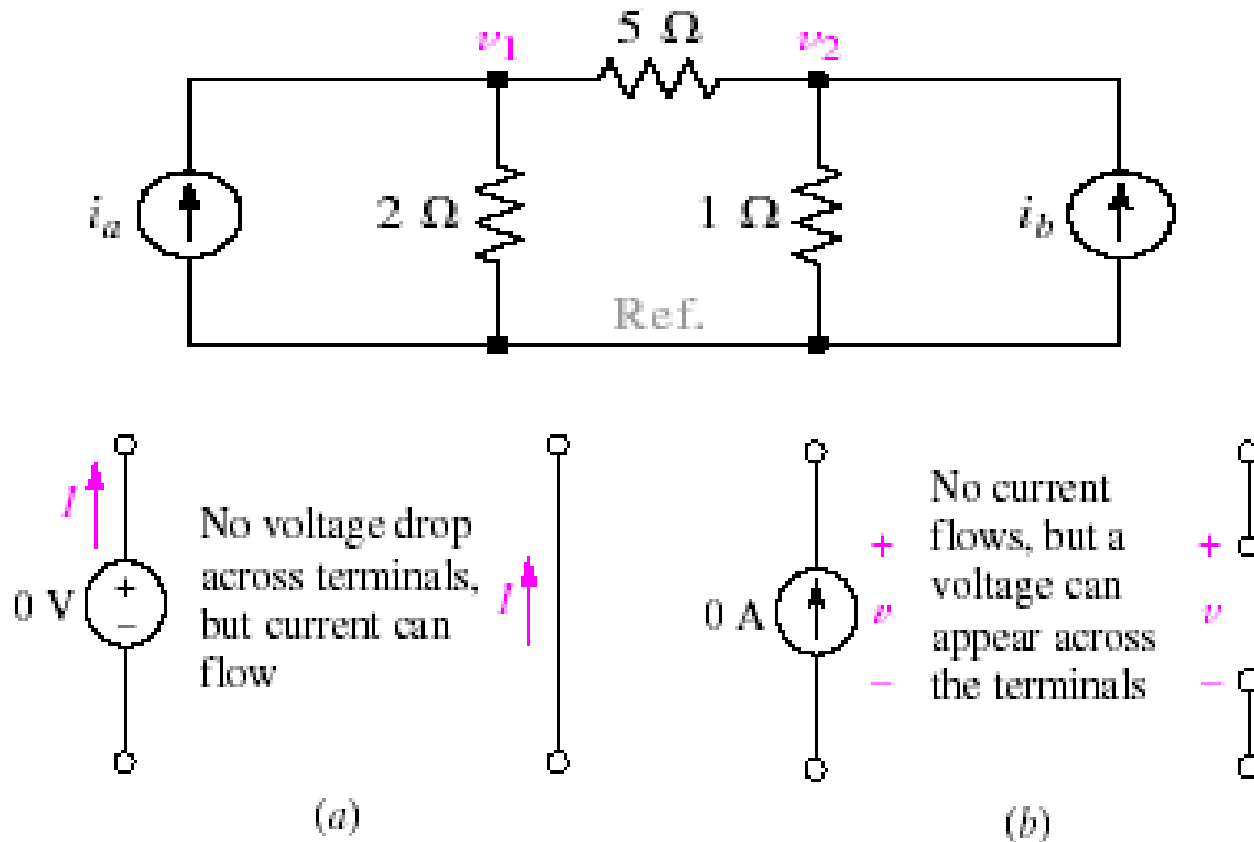- Use **superposition principle** 叠加原理 to analyzed circuit




Remove power principle 除源原则

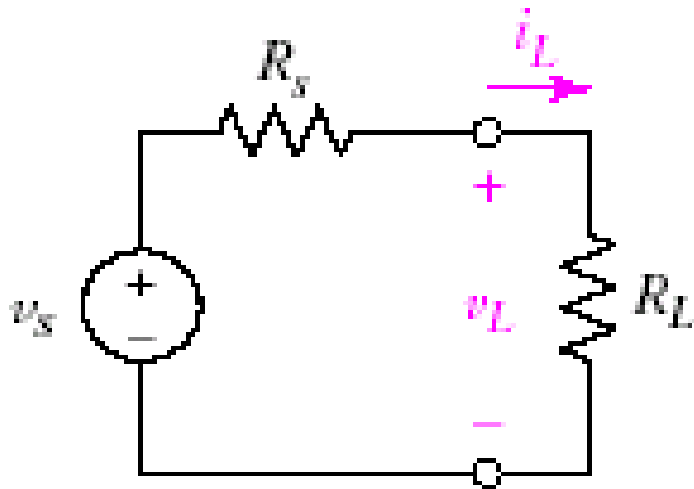- Use **source transformations** 电源变换 to reduce the complexity of a circuit.



(a)

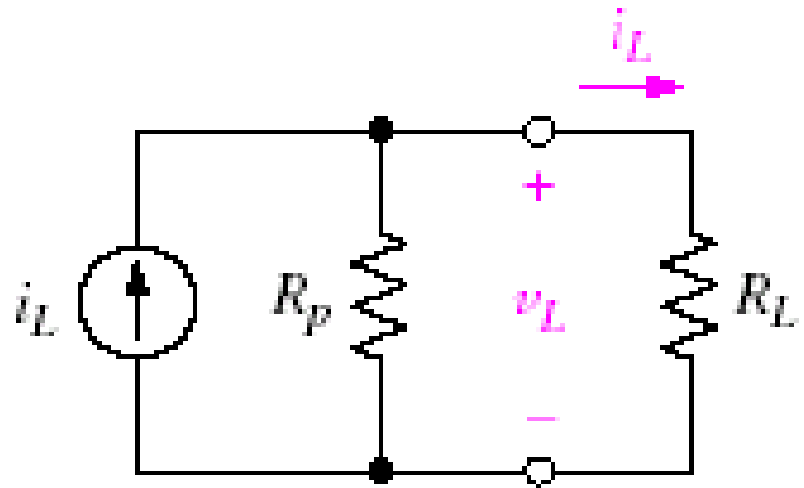

(b)


$$R_s = R_p$$

$$v_s = R_p i_s = R_s i_s$$

A few parting comments:

- When performing a source transformation, remember that the **head of the current source arrow** corresponds to the “+” **terminal of the voltage source**. [注意变换前后电源方向]
- If the voltage or current associated with a particular resistor is used in a controlling variable for a dependent source, or is the desired response of a circuit, the resistor should not be included in source transformations. [受控源控制量和待求量不要被变没了！]
- In using source transformations, one common goal is to end up with either all current sources or all voltage sources in the final circuit whenever possible. [为方便计算，可全部变为同一种电源]
- Repeated source transformations can be used to simplify a circuit by allowing resistors and sources to be combined. [用电源等效变换化简电路过程中，可结合电阻、电源串并联组合的方法]

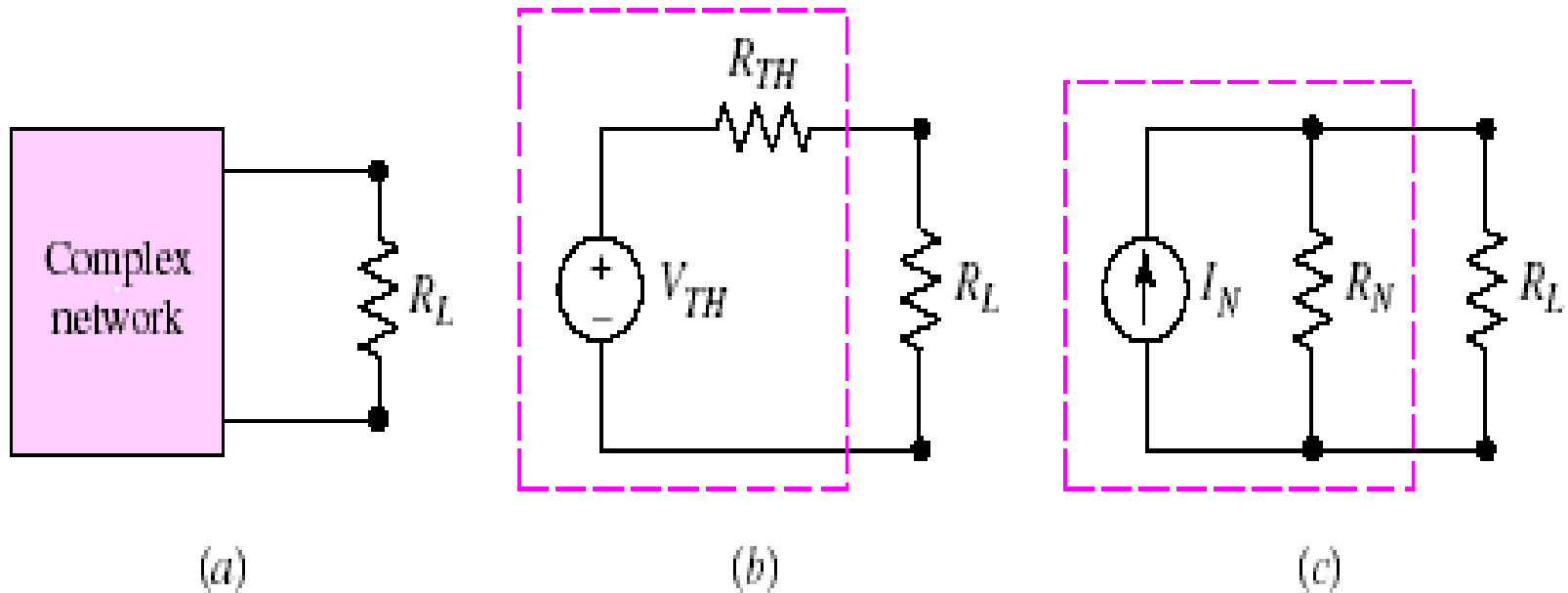- Determine the **Thévenin and Norton equivalent Circuits** 戴维宁和诺顿等效网络 of any network




(a) A complex network including a load resistor R_L . (b) A Thévenin equivalent network connected to the load resistor R_L . (c) A Norton equivalent network connected to the load resistor R_L .

$$v_{oc} = R_{TH} i_{sc}$$

- Compute the load resistance that will result in maximum power transfer. 计算产生最大功率传输的负载电阻
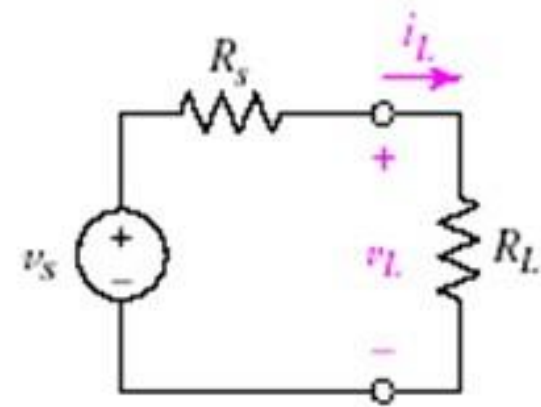
$$p_L = i_L^2 R_L = \frac{v_s^2 R_L}{(R_s + R_L)^2}$$



maximum

$$R_s = R_L$$

Chapter 5 Capacitors and Inductors

$$i = C \frac{dv}{dt}$$

$$v = L \frac{di}{dt}$$

where v and i satisfy the conventions for a passive element

Inductors in Series

$$L_{eq} = (L_1 + L_2 + \Lambda + L_N)$$

Capacitors in Series

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

Inductors in Parallel




$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

Capacitors in Parallel

$$C_{eq} = C_1 + C_2 + \Lambda + C_N$$

Chapter 6 Basic RL and RC Circuits

- A circuit reduced to a single equivalent inductance L and a single equivalent resistance R will have a natural response given by $i(t) = I_0 e^{-t/\tau}$, where $\tau = L/R$ is the circuit time constant.
- A circuit reduced to a single equivalent capacitance C and a single equivalent resistance R will have a natural response given by $v(t) = V_0 e^{-t/\tau}$, where $\tau = RC$ is the circuit time constant.

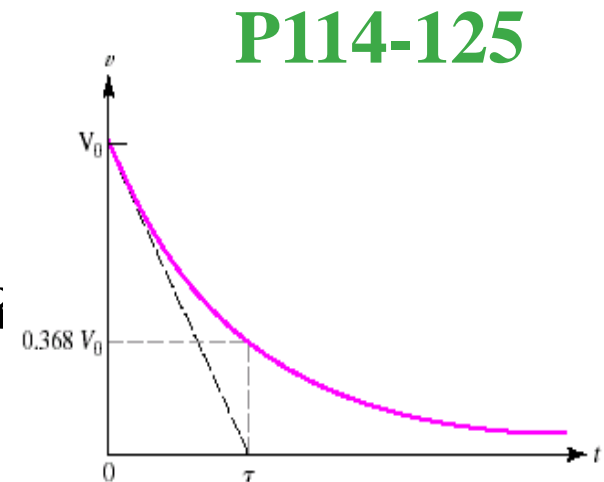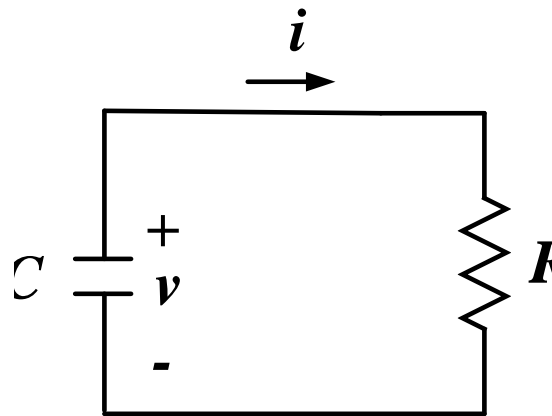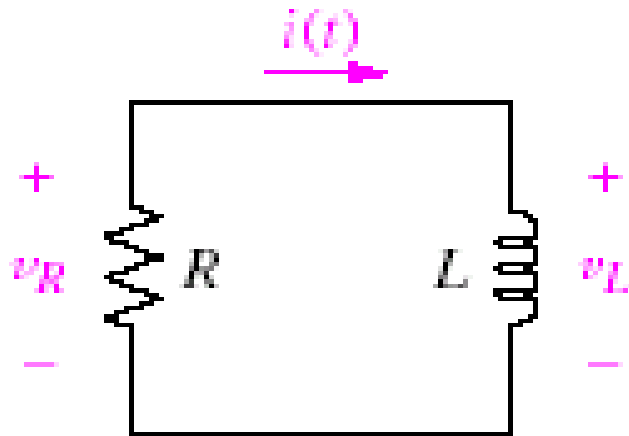

- Calculation of the **total response** of RL and RC circuits

complete response = forced response + natural response

The **forced response** is thus obtained by inspection of the final circuit.

用分析电路的方法得到强迫相应（稳态解）

The form of the **natural response** (also referred to as the transient response) depends only on the component values and the way they are wired together.

自由响应与原件性质参数和连接关系有关


$$i = i_n + i_f$$

$$i_n = Ae^{-Rt/L}$$

$$i_f = V_0 / R$$

$$i = Ae^{-Rt/L} + V_0 / R$$

$$0 = A + V_0 / R$$

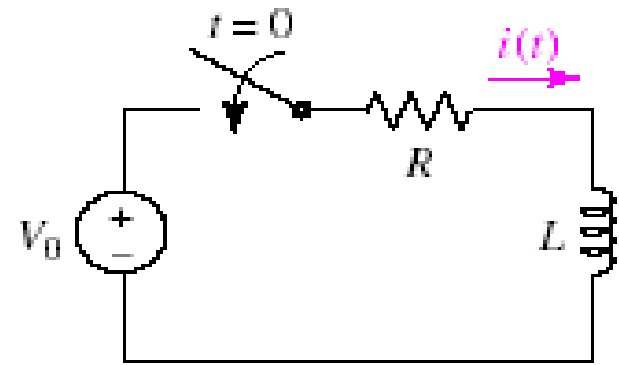

$$i = (1 - e^{-Rt/L})V_0 / R$$

P132-135

$$f(t) = f(\infty) + Ae^{-t/\tau}$$

$$f(0^+) = f(\infty) + A$$

$$f(t) = f(\infty) + [f(0^+) - f(\infty)]e^{-t/\tau}$$

total response = final value + (initial value – final value) $e^{-t/\tau}$

Chapter 7 Sinusoidal Steady-State Analysis

- If two sine waves (or two cosine waves) both have positive magnitudes and the same frequency, it is possible to determine which waveform is **leading** and which is **lagging** by comparing their phase angles.

判断两个正弦信号的相位关系。

$$v(t) = V_m \sin(\omega t + \theta)$$

- The forced response of a linear circuit to a sinusoidal voltage or current source can always be written as a single sinusoid having **the same frequency** as the sinusoidal source.

线性电路中正弦激励的稳态响应（强迫响应）是**同频率**的正弦信号。

- A phasor transform may be performed on any sinusoidal function. A phasor has both **a magnitude** and **a phase angle**; the frequency is understood to be that of the sinusoidal source driving the circuit.

向量法在正弦信号中的应用。

$$i(t) = I_m \cos(\omega t + \phi) \quad \longrightarrow$$


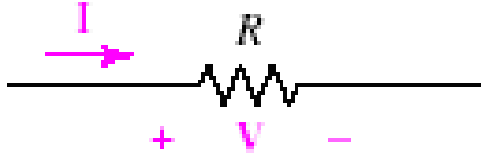
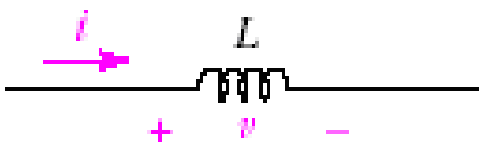

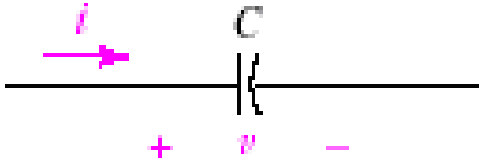

$$\dot{I} = I_m \angle \phi$$

Phasor Diagrams 向量图法

- When transforming a time-domain circuit into the corresponding frequency-domain circuit, resistors, capacitors, and inductors are replaced by impedances (or, occasionally by admittances).

用向量法将时域电路转为频域电路时，电阻、电容、电感都要转换为阻抗（或导纳）。

- The impedance of a resistor is simply its resistance.
- The impedance of a capacitor is $1/j\omega C$.
- The impedance of an inductor is $j\omega L$.

Time domain	Frequency domain		
	$v = Ri$	$V = RI$	
	$v = L \frac{di}{dt}$	$V = j\omega LI$	
	$v = \frac{1}{C} \int i dt$	$V = \frac{1}{j\omega C} I$	

- Impedance combine both in series and in parallel combinations in the same manner **as resistors**.

阻抗(导纳)的串并联计算

P162-166 7.7 Impedance

P166-167 7.8 Admittance

- **All analysis techniques** previously used on resistive circuits apply to circuits with capacitors and/or inductors once all elements are replaced by their frequency-domain equivalents.

频域电路（用向量法描述的电路）计算方法

P167-169 7.9 Nodal and Mesh Analysis

Chapter 8 AC Circuit Power Analysis

- Defining the **average power** 平均功率 supplied by a sinusoidal source. (P183-188)

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

- Average Power Absorbed by an **Ideal Resistor**

$$P_R = \frac{1}{2} V_m I_m \cos 0 = \frac{1}{2} V_m I_m$$

$$P_R = \frac{1}{2} I_m^2 R$$

$$P_R = \frac{V_m^2}{2R}$$

- Average Power Absorbed by **Purely Reactive Elements**

$$P_R = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

- Calculating the **rms** 均方根/有效值 value of a time-varying waveform.


$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

root-mean-square

Use of RMS values to compute average power. P192-193

$$I_{eff} = I_m / \sqrt{2}$$

$$P = \frac{1}{2} I_m^2 R$$

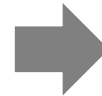

$$P = I_{eff}^2 R$$

$$V_{eff} = V_m / \sqrt{2}$$

$$P = \frac{V_m^2}{2} R$$



$$P = \frac{V_{eff}^2}{R}$$

$$P = V_{eff} I_{eff} \cos(\theta - \phi)$$

- Apparent Power and Power Factor 视在功率和功率因数(P194)

$$v = V_m \cos(\omega t + \theta)$$


$$i = I_m \cos(\omega t + \phi)$$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

$$P = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$\text{PF} = \frac{\text{average power}}{\text{apparent power}} = \frac{P}{V_{off} I_{off}} = 0 \sim 1$$

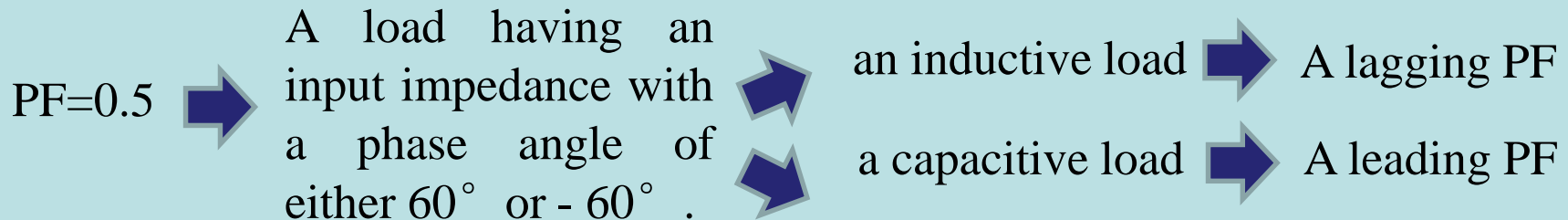- Identifying the **power factor** 功率因数 of a given load, and learning means of improving it. (P195-196)





- Using complex power to identify **average** 有功功率 **and reactive power** 无功功率.

The complex power is defined as $S=P+jQ$, or $S=V_{\text{eff}}I_{\text{eff}}^*$. It is measured in units of volt-amperes (VA).

$$S = V_{\text{eff}} I_{\text{eff}}^* = P + jQ$$
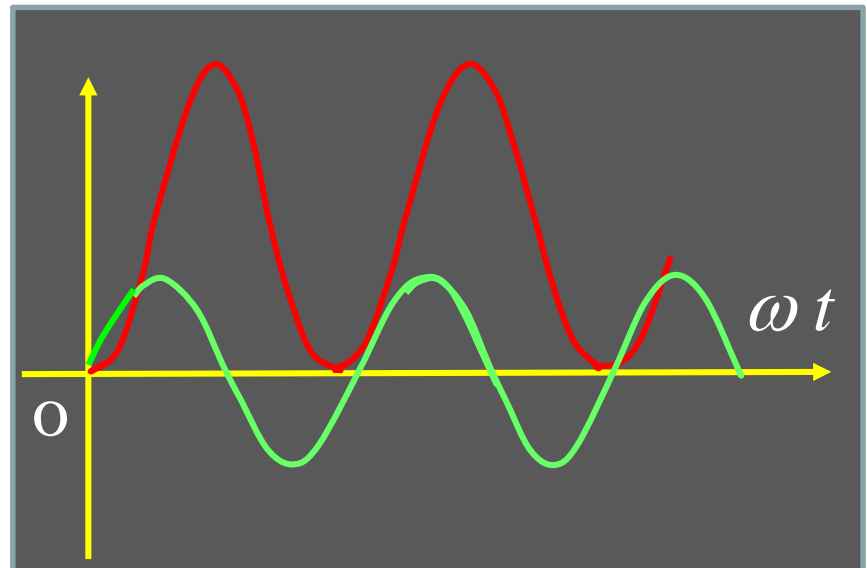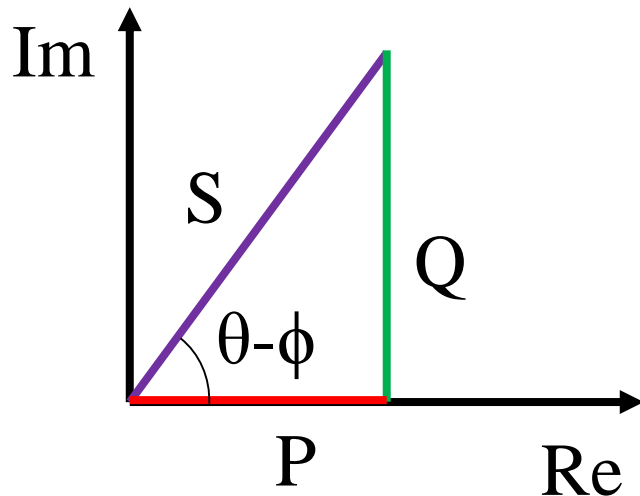
$$Q = V_{\text{eff}} I_{\text{eff}} \sin(\theta - \phi)$$





$$p(t) = \frac{1}{2} V_m I_m \cos(\theta - \phi) (1 + \cos(2\omega t + 2\theta)) + \frac{1}{2} V_m I_m \sin(2\omega t + 2\theta) \sin(\theta - \phi)$$

Comparison of Power Terminology P199



Term	Symbol	Unit	Description
Instantaneous power	$p(t)$	w	$p(t)=v(t)i(t)$. It is the value of the Power at a specific instant in time. It is not the product of the voltage and current phasors.
Average power	P	w	In the sinusoidal steady state, $P= \frac{1}{2} V_m I_m \cos(\theta-\phi)$, where θ is the voltage phase angle, and ϕ is the phase angle of the current. Reactances do not contribute to P.
Effective or RMS value	V_{rms} or I_{rms}	V or A	Defined as $I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$; if $i(t)$ is sinusoidal, then $I_{eff} = I_m / \sqrt{2}$
Apparent power	$ S $	VA	$ S = V_{eff} I_{eff}$, and is the maximum value the average power can be; $P= S $ only for purely resistive loads.
Power factor	PF(or λ or $\cos\phi$)	None	Ratio of the average dissipated power to the apparent power. The PF is unity for a purely resistive load, and zero for a purely reactive load.
Reactive power	Q	VAR	A means of measuring the energy flow rate to and from reactive loads.
Complex power	S	VA	A convenient complex quantity that contains both the average power P and the reactive power Q: $S=P+jQ$

Chapter 9 Polyphase Circuits

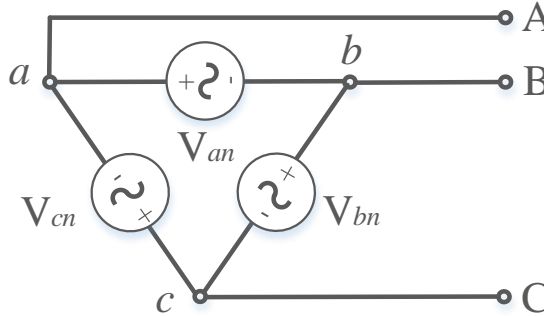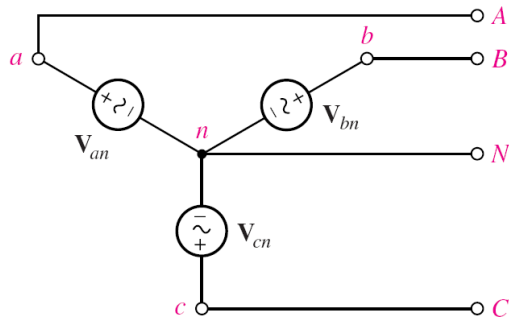- Three phase sources can be either **Y** or **Δ** connected.
- In a **balanced three-phase** system, each phase voltage has the same magnitude, but is 120° out of phase with the other two.


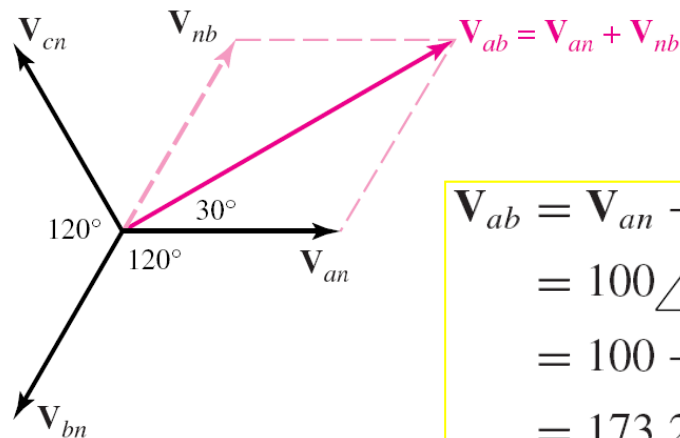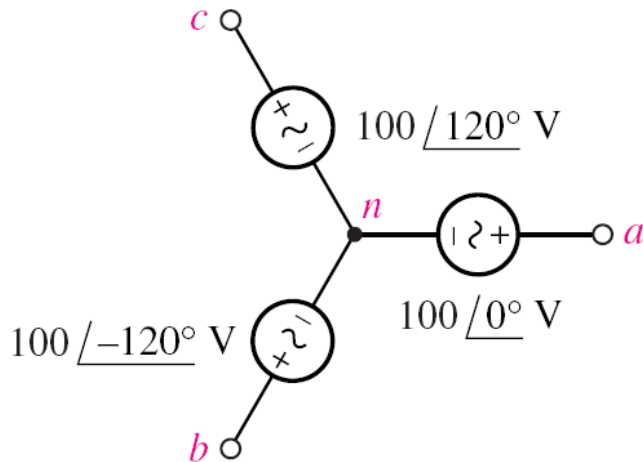
$$\begin{aligned} V_{an} &= 100 \angle 0^\circ \text{ V} \\ V_{bn} &= 100 \angle -120^\circ \text{ V} \\ V_{cn} &= 100 \angle -240^\circ \text{ V} \end{aligned}$$



(P209-211)

$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} = V_{an} - V_{bn} \\ &= 100 \angle 0^\circ - 100 \angle -120^\circ \text{ V} \\ &= 100 - (-50 - j86.6) \text{ V} \\ &= 173.2 \angle 30^\circ \text{ V} \end{aligned}$$

- These three voltages, each existing between one line and the neutral, are called **phase voltages** 相电压. (P215)

$$\mathbf{V}_{an} = V_p \angle 0^\circ$$

$$\mathbf{V}_{bn} = V_p \angle -120^\circ$$



$$\mathbf{V}_{cn} = V_p \angle -240^\circ$$

- These line-to-line voltages are often simply called the **line voltages** 线电压. (P216)


$$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$$

$$\mathbf{V}_{bc} = \sqrt{3}V_p \angle -90^\circ$$
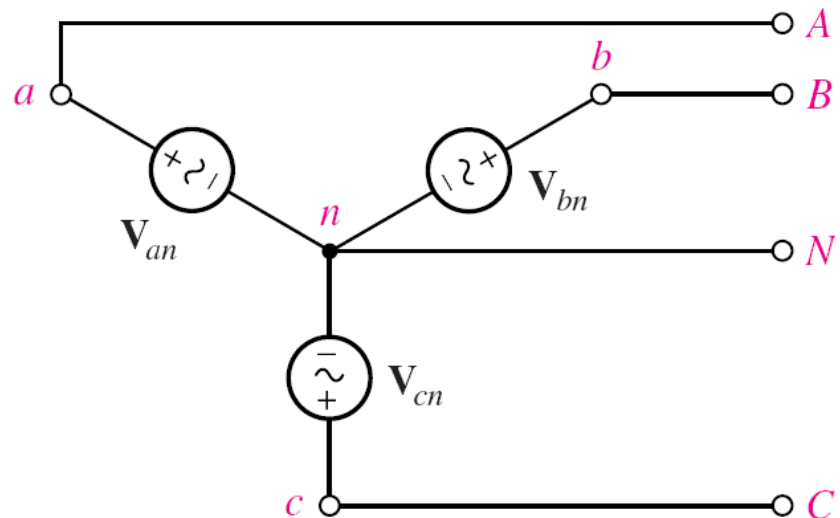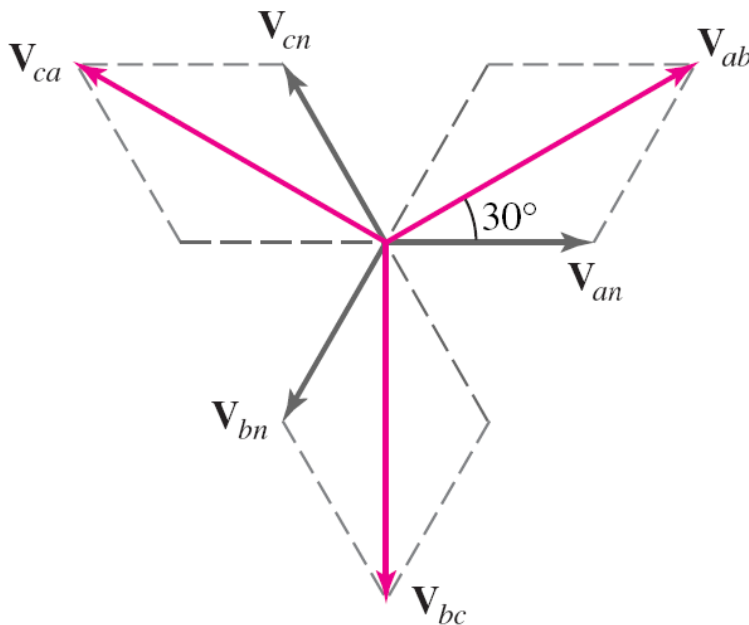
$$\mathbf{V}_{ca} = \sqrt{3}V_p \angle -210^\circ$$



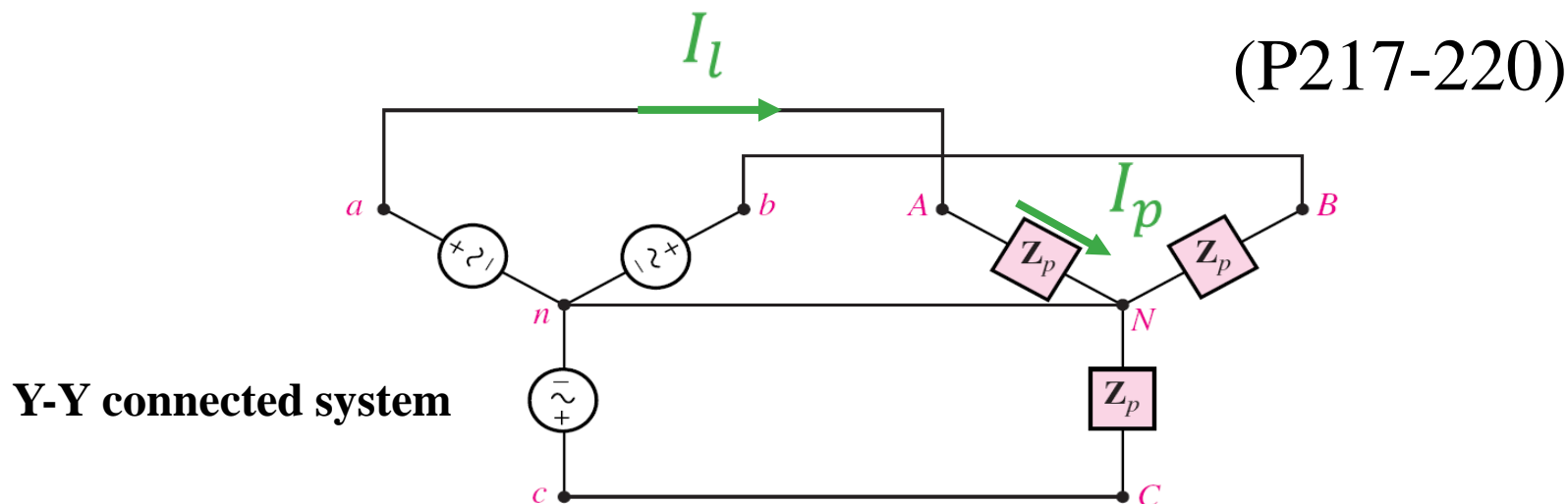- Loads in three-phase system may be either Y or Δ connected. In a Y-connected load, the line currents are equal to the phase currents.



$$\dot{V}_{AB} = \sqrt{3} \dot{V}_{AN} \angle 30^\circ$$

$$\dot{I}_{aA} = \dot{I}_{AN} = \dot{V}_{AN} / Z_p$$



$$|\dot{V}_{AB}| = |\dot{V}_{ab}| = \dot{V}_l \quad |V_{AN}| = V_p \quad |\dot{I}_{aA}| = I_l \quad |\dot{I}_{AN}| = I_p$$

$$V_l = \sqrt{3} V_p$$

$$I_l = I_p$$

$$P_\Sigma = 3P_p = 3V_p I_p \cos \theta_{Z_p} = \sqrt{3} V_l I_l \cos \theta_{Z_p}$$

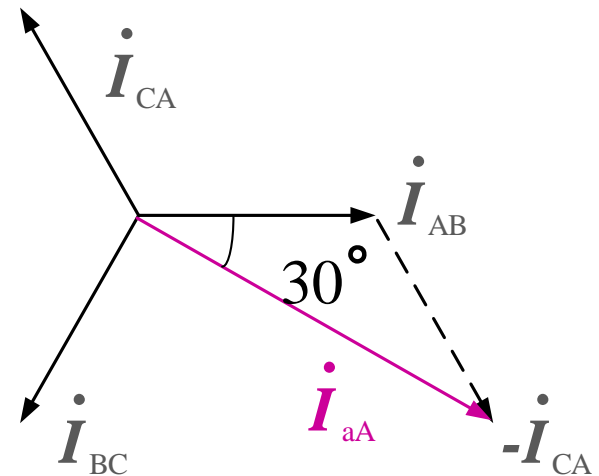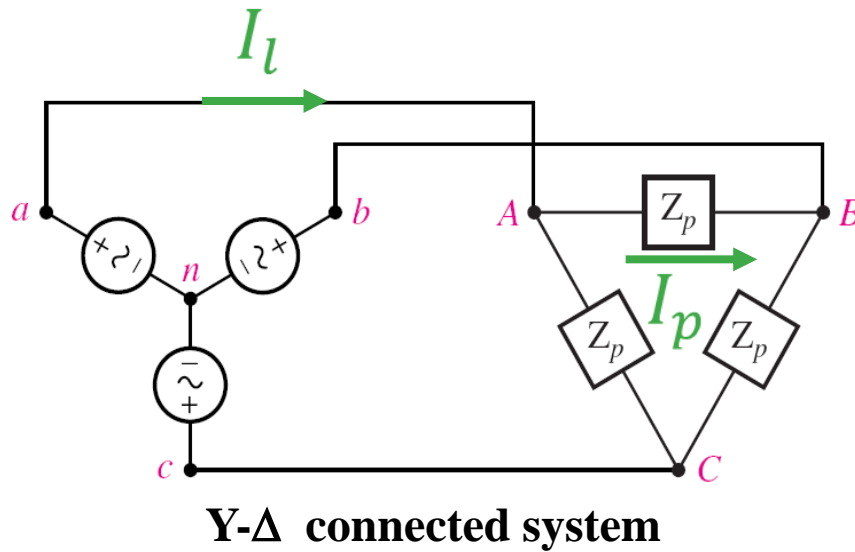- In a Δ -connected load, the line voltages are equal to the phase voltages.



$$\dot{V}_{AB} = \dot{V}_{ab}$$

$$|\dot{V}_{ab}| = V_l \quad |\dot{V}_{AB}| = V_p$$

$$V_l = V_p$$

$$\dot{I}_{aA} = \dot{I}_{AB} - \dot{I}_{CA} = \sqrt{3} \dot{I}_{AB} \angle -30^\circ$$

$$\dot{I}_{AB} = \dot{V}_{AB} / Z_p$$

$$|\dot{I}_{aA}| = I_l \quad |\dot{I}_{AB}| = I_p$$

$$I_l = \sqrt{3} I_p$$

$$P_\Sigma = 3P_p = 3V_p I_p \cos \theta_{Z_p} = \sqrt{3} V_l I_l \cos \theta_{Z_p}$$